

WORKSHEET

Parallel P9

Student Name _____ date _____ MB# _____

Students should be able to Calculate, Measure and Compare fundamental characteristics of a parallel circuit.

- **Measure (A):** The student will use a Digital Multimeter (DMM), to measure the current (I), voltage (E), and resistance (R) for the Circuit on the P9 circuit on the Miniboard Parallel Trainer (simulator).
- **Calculate(B):** The student will use the principles of ohms law to calculate, current (I), voltage (E), and resistance (R) for the P9 Circuit using the measurements taken with the DMM on the Miniboard Parallel Trainer (simulator) Part A above.
- **Compare (C):** The student will then compare the results of the measurements taken and those calculated.

Part A Measure

Measuring Voltages:

Measure and record Battery Voltage

a _____

Measure and record Total Voltage Drop for Parallel circuit P9

b _____

Measuring Resistance:

Measure and Record total resistance (Rt) of circuit P9

c _____

Measuring Amperage:

Measure and Record the total amperage of circuit P9

d _____

Part B Calculate

Calculate Resistance Total for circuit P9

(E / I)

Using the value of the resistors according to color code bands, or the instructor might supply resistance values to the student. (measuring individual resistance values with a DMM are not possible in a Parallel circuit for this reason another method must be used to find individual resistance values) Using the formulas of ohms law to calculate total resistance in a parallel circuit.

Calculate the total Resistance for circuit P9 by using resistor values for all resistors

R1 resistance (circle one color bands or provided)

e _____

R2 resistance (circle one color bands or provided)

f _____

R3 resistance (circle one color bands or provided)

g _____

R4 resistance (circle one color bands or provided)

h _____

Calculate P6 resistance total (Rt) using parallel formulas

i _____

Calculate Amperage (E / R) = I

Current flow through any resistor is dependent on the resistance of the resistor. Therefore it must be calculated for each resistor by multiplying resistance of the individual resistor by the total amperage for the circuit (It). Then sum the amperage's for each resistor, to obtain total amperage for that circuit (It) for P9.

Calculate amperage for:

R1 amperage	(b / e)	j _____
R2 amperage	(b / f)	k _____
R3 amperage	(b / g)	l _____
R4 amperage	(b / h)	m _____
P9 Amperage Sum Total	sum	n _____
Calculate P9 total amperage	(b/c)	o _____

Since the amperage has been calculated for R1, R2, R3 and 3R4 resistance can be calculated for R1, R2,R3 and R4 :

Calculate the resistance for R1	(b / j)	p _____
Calculate the resistance for R2	(b / k)	q _____
Calculate the resistance for R3	(b / l)	r _____
Calculate the resistance for R4	(b / I)	s _____

Calculate Voltage (R X I)

Calculate P9 total Voltage Drop	(c x d)	t _____
---------------------------------	---------	---------

Part C Compare

Record measured and calculated results to complete the following table. Note: letters in each cell refer to your answers above. (Measured and calculated readings should be less than + - 5%)

Voltages	Measured	Calculated	< 5% Difference Y / N
P9 Voltage Drop (Et)	b	t	
Resistance	Measured	Calculated	
	circle one		
R1 resistance	e /Bands or Provided	p	
R2 resistance	f /Bands or Provided	q	
R3 resistance	g /Bands or Provided	r	
R4 resistance	h /Bands or Provided	s	
P9 resistance total (Rt)	c	i	
Amperage	Measured	Calculated	
R1 amperage	NA	j	NA
R2 amperage	NA	k	NA
R3 amperage	NA	l	NA
R4 amperage	NA	m	Amperage Sum NA
P9 amperage total (It)	d	o	n