

# WORKSHEET

## Parallel P6

Student Name \_\_\_\_\_ date \_\_\_\_\_ MB# \_\_\_\_\_

Students should be able to Calculate, Measure and Compare fundamental characteristics of a parallel circuit.

- **Measure (A):** The student will use a Digital Multimeter (DMM), to measure the current (I), voltage (E), and resistance (R) for the Circuit on the P6 circuit on the Miniboard Parallel Trainer (simulator).
- **Calculate(B):** The student will use the principles of ohms law to calculate, current (I), voltage (E), and resistance (R) for the P6 Circuit using the measurements taken with the DMM on the Miniboard Parallel Trainer (simulator) Part A above.
- **Compare (C):** The student will then compare the results of the measurements taken and those calculated.

### Part A Measure

#### Measuring Voltages:

Measure and record Battery Voltage

a \_\_\_\_\_

Measure and record Total Voltage Drop for Parallel circuit P6

b \_\_\_\_\_

#### Measuring Resistance:

Measure and Record total resistance (Rt) of circuit P6

c \_\_\_\_\_

#### Measuring Amperage:

Measure and Record the total amperage of circuit P6

d \_\_\_\_\_

### Part B Calculate

#### Calculate Resistance Total for circuit P6 (E / I)

Using the value of the resistors according to color code bands, or the instructor might supply resistance values to the student. (measuring individual resistance values with a DMM are not possible in a Parallel circuit for this reason another method must be used to find individual resistance values) Using the formulas of ohms law to calculate total resistance in a parallel circuit.

#### Calculate the total Resistance for circuit P6 by using resistor values for all resistors

R1 resistance (circle one color bands or provided)

e \_\_\_\_\_

R2 resistance (circle one color bands or provided)

f \_\_\_\_\_

R3 resistance (circle one color bands or provided)

g \_\_\_\_\_

R4 resistance (circle one color bands or provided)

h \_\_\_\_\_

Calculate P6 resistance total (Rt) using parallel formulas

i \_\_\_\_\_

#### Calculate Amperage (E / R) = I

*Current flow through any resistor is dependent on the resistance of the resistor. Therefore it must be calculated for each resistor by multiplying resistance of the individual resistor by the total amperage for the circuit (It). Then sum the amperage's for each resistor, to obtain total amperage for that circuit (It) for P6.*

**Calculate amperage for:**

R1 amperage	(b / e)	j _____
R2 amperage	(b / f)	k _____
R3 amperage	(b / g)	l _____
R4 amperage	(b / h)	m _____
P6 Amperage Sum Total	sum	n _____
Calculate P6 total amperage	(b/c)	o _____

**Since the amperage has been calculated for R1, R2, R3 and 3R4 resistance can be calculated for R1, R2,R3 and R4 :**

Calculate the resistance for R1	(b / j)	p _____
Calculate the resistance for R2	(b / k)	q _____
Calculate the resistance for R3	(b / l)	r _____
Calculate the resistance for R4	(b / I)	s _____

**Calculate Voltage (R X I)**

Calculate P6 total Voltage Drop	(c x d)	t _____
---------------------------------	---------	---------

**Part C Compare**

Record measured and calculated results to complete the following table. Note: letters in each cell refer to your answers above. (Measured and calculated readings should be less than + - 5%)

<b>Voltages</b>	<b>Measured</b>	<b>Calculated</b>	<b>&lt; 5% Difference Y / N</b>
P6 Voltage Drop (Et)	b	t	
<b>Resistance</b>	<b>Measured</b>	<b>Calculated</b>	
R1 resistance	e /Bands or Provided	p	
R2 resistance	f /Bands or Provided	q	
R3 resistance	g /Bands or Provided	r	
R4 resistance	h /Bands or Provided	s	
P6 resistance total (Rt)	c	i	
<b>Amperage</b>	<b>Measured</b>	<b>Calculated</b>	
R1 amperage	NA	j	NA
R2 amperage	NA	k	NA
R3 amperage	NA	l	NA
R4 amperage	NA	m	Amperage Sum NA
P6 amperage total (It)	d	o	n